
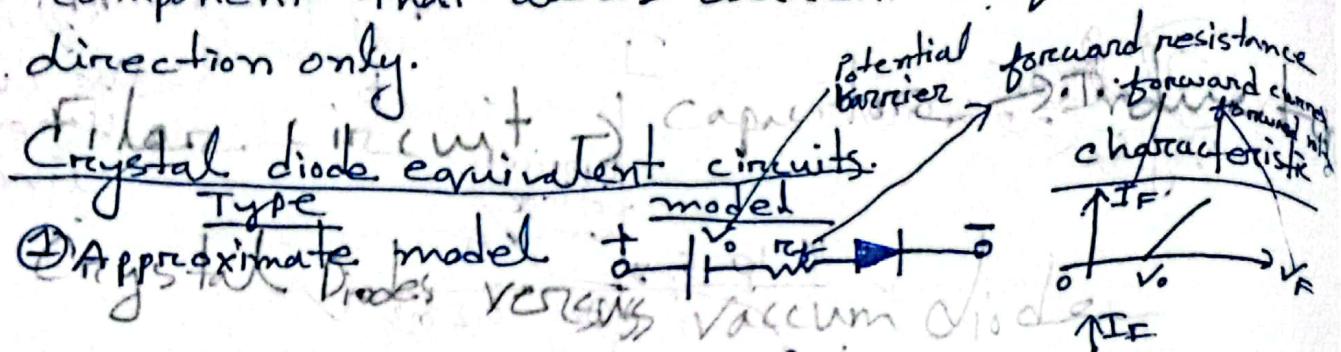


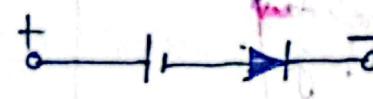
Crystal diode: A crystal diode, also known as a semiconductor diode, is a type of electronic component that allows current to flow in one direction only.



② Simplified model



③ Ideal model

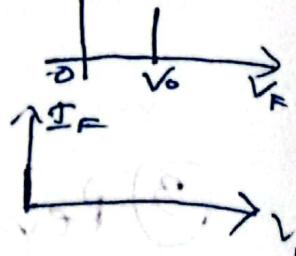

i) Forward current: It is the current that flows through a forward biased diode.


ii) Peak inverse voltage: It is the maximum reverse voltage that a diode can withstand without destroying the junction.

iii) Reverse current / leakage current: It is the current that flows through a reversed biased diode.

### Half-Wave Rectifier

In a half-wave rectifier, the rectifier conducts current only during the positive half-cycles of input ac supply. During negative half-cycles, no current is conducted and hence no voltage

is c-appears across the Lead.


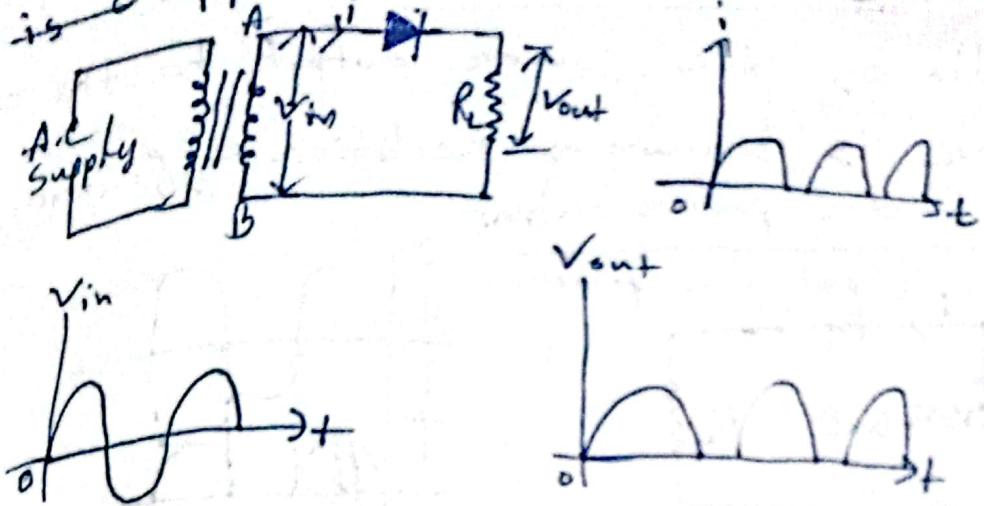


Operation: The a.c voltage across the secondary winding AB changes polarities after every half-cycle. During the positive half-cycle of input a.c voltage, end A becomes positive w.r.t end B. This makes the diode forward biased and it conducts current. During the negative half-cycle, of input end A becomes negative w.r.t. end B. This makes the diode reverse biased and it conducts no current. Therefore the current flows only positive half-cycle of input a.c voltage only. Current flows through load  $R_L$ . Hence dc output across  $R_L$  is obtained across  $R_L$ .
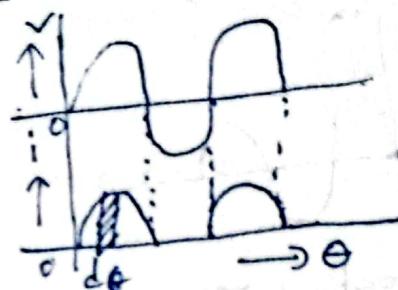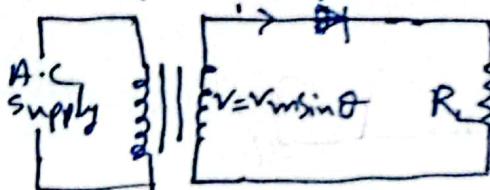
## Efficiency of Half-Wave Rectifier:

The ratio of d.c. power output to the input ac power is known as rectifier efficiency.

$$\eta = \frac{\text{d.c. power output}}{\text{input a.c. power}}$$



d.c. power output: The output current is pulsating dc current.

$$I_{dc} = \frac{1}{2\pi} \int_0^\pi i d\theta = \frac{1}{2\pi} \int_0^\pi \frac{V_m \sin \theta}{R_L + r_f} d\theta = \frac{V_m}{2\pi(R_L + r_f)} \left[ -\cos \theta \right]_0^\pi = \frac{V_m}{2\pi(R_L + r_f)}$$

$$= \frac{V_m}{2\pi(r_f + R_L)} [ -\cos \pi - (-\cos 0) ] = \frac{V_m}{2\pi(r_f + R_L)} \times 2 = \frac{V_m}{r_f + R_L}$$

$$= \frac{I_m}{\pi} \quad \left[ \because I_m = \frac{V_m}{r_f + R_L} \right]$$

$\therefore$  d.c. power

$$P_{dc} = I_{dc} \times R_L = \left( \frac{I_m}{\pi} \right) \times R_L$$

a.c. power input:

$$P_{ac} = I_{rms} \times (r_f + R_L)$$

$$\therefore P_{ac} = \left( \frac{I_m}{2} \right)^2 \times (r_f + R_L) \quad \left[ \text{For a half wave rectifier wave, } I_{rms} = \frac{I_m}{2} \right]$$

$$\therefore \text{Rectifier efficiency} = \frac{\text{d.c. output power}}{\text{a.c. input power}} = \frac{\left( \frac{I_m}{\pi} \right) \times R_L}{\left( \frac{I_m}{2} \right)^2 (r_f + R_L)}$$

$$= \frac{0.406 R_L}{r_f + R_L} = \frac{0.406}{1 + \frac{r_f}{R_L}}$$



The efficiency will be maximum if  $r_f$  is negligible as compared to  $R_L$ .

$\therefore$  Max. rectifier efficiency = 40.6%.

### full wave rectifier:

In a full wave rectification, the rectifier conducts current only during the positive and negative half both half-cycle of input ac supply.


### i) centre-tap full-wave rectifier:

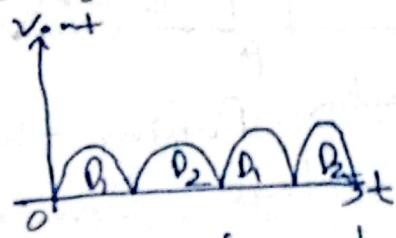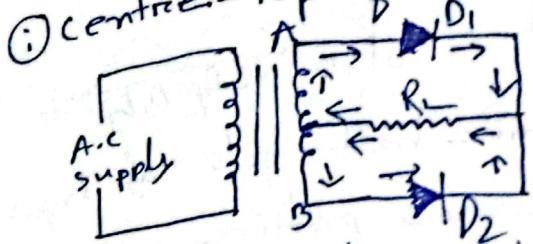


Operation: During the positive half-cycle of input ac voltage, end A becomes positive w.r.t end B. This makes the diode  $\neq D_1$  forward biased and Diode  $D_2$  reverse biased. Therefore, diode  $D_1$  conducts while diode  $D_2$  does not. During the negative half-cycle, end A becomes negative w.r.t end B. This makes the diode  $D_1$  reverse biased and Diode  $D_2$  forward biased. Therefore diode  $D_2$  conducts while diode  $D_1$  does not. It may be seen that current in the load  $R_L$  is in the same direction for both half-cycle of input a.c voltage. D.c is obtained across the load.
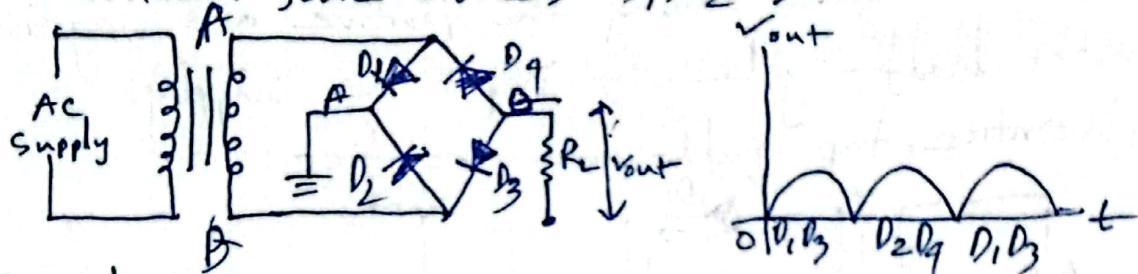
## ⑪ Full-wave Bridge Rectifier:

It contains four diodes  $D_1, D_2, D_3$  and  $D_4$ .




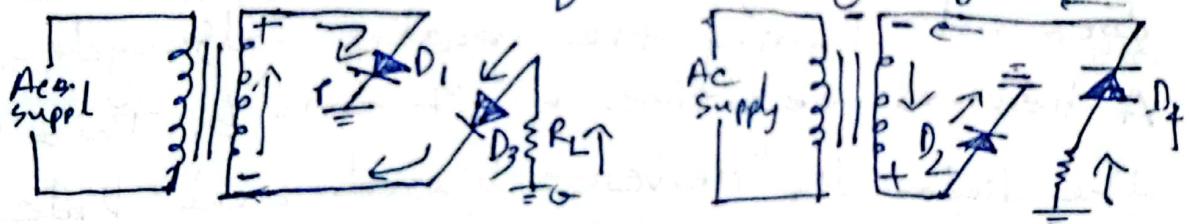Operation: During the positive half-cycle of input ac voltage, end A becomes positive w.r.t. end B. This makes the diode  $D_1$  and  $D_3$  forward biased while diode  $D_2$  and  $D_4$  are reverse biased. Therefore, only diode  $D_1$  and  $D_3$  conduct. Current flows from A to B through the load.



During the negative half-cycle, end A becomes negative w.r.t. end B. This makes the diode  $D_1$  and  $D_3$  reverse biased and  $D_2$  and  $D_4$  are forward biased. Therefore, only diode  $D_2$  and  $D_4$  conduct current. Therefore, dc output is obtained across load resistor  $R_L$ .

## Efficiency of Full-wave Rectifier:

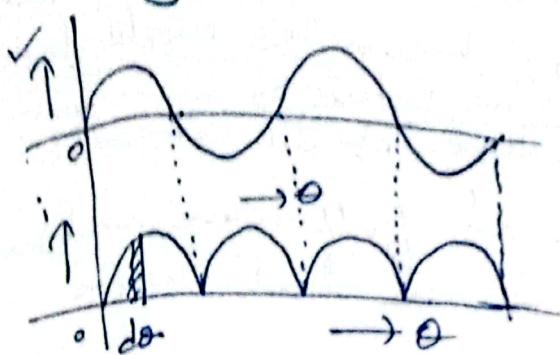

dc output power: The output current is pulsating dc current. From the knowledge of electrical engineering.

$$I_{dc} = \frac{2Im}{\pi}$$

∴ dc power output,  $P_{dc} = I_{dc} \times R_L = \left(\frac{2Im}{\pi}\right)^2 \times R_L$

ac power input:

$$P_{ac} = I_{rms}^2 (r_f + R_L)$$

$$P_{ac} = \left(\frac{Im}{\sqrt{2}}\right)^2 (r_f + R_L)$$

For a full wave rectified wave, we have  $I_{rms} = \frac{Im}{\sqrt{2}}$

∴ efficiency is  $\eta = \frac{P_{dc}}{P_{ac}} = \frac{\left(\frac{2Im}{\pi}\right)^2 \times R_L}{\left(\frac{Im}{\sqrt{2}}\right)^2 (r_f + R_L)}$

$$= \cancel{\frac{2}{\pi^2}} \times \frac{R_L}{(r_f + R_L)} = \frac{0.812 R_L}{r_f + R_L}$$

∴ Maximum efficiency is  $= 81.2\%$ .

This is double the efficiency due to half-wave rectifier. Therefore, a ~~half~~ <sup>full</sup> wave is twice as effective as a half-wave rectifier.

it is very important in deciding the effectiveness of a rectifier

Ripple Factor: The ratio of r.m.s value of a.c component to the d.c component in the rectifier output is known as ripple factor.

Ripple factor =  $\frac{\text{r.m.s value of a.c component}}{\text{value of d.c component}} = \frac{I_{ac}}{I_{dc}}$

Q1 The ripple factor of full-wave rectification is less than that of the half-wave rectification.

For half-wave rectification:

$$I_{rms} = \frac{Im}{2} \quad I_{dc} = \frac{Im}{\pi}$$

$$\therefore \text{Ripple factor} = \sqrt{\left(\frac{I_{rms}}{I_{dc}}\right)^2 - 1} = \sqrt{\left(\frac{Im/2}{Im/\pi}\right)^2 - 1} = 1.21$$

This means that in half-wave rectification, the A.C component is larger than the D.C component.

For Full-wave Rectification:

$$I_{rms} = \frac{\pi Im}{\sqrt{2}} \quad I_{dc} = \frac{2 Im}{\pi}$$

$$\therefore \text{Ripple factor} = \sqrt{\left(\frac{I_{rms}}{I_{dc}}\right)^2 - 1} = \sqrt{\left(\frac{Im\pi/2}{2 Im/\pi}\right)^2 - 1} = 0.48$$




This means in the output of a full-wave rectifier, the D.C component is more than the A.C component. Finally, the ripple factor of full wave rectification is less than that of the half-wave rectification.

Filter circuit: A filter circuit is a device which removes the a.c. component of rectifier output but allows the d.c. component to reach the load.


Q) Describe the action of the following filter circuit: i) capacitor filter ii) choke input filter iii) capacitor input filter

Ans  
Capacitor filter:

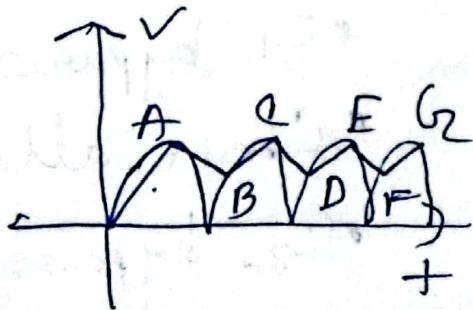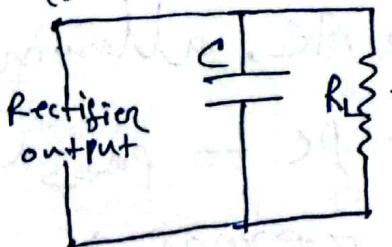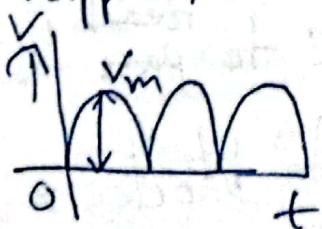A capacitor is connected across the rectifier output in parallel with the load. The pulsating dc voltage from the rectifier charges the capacitor. As the rectifier voltage increases, the capacitor charges, and as the rectifier voltage decreases, the capacitor discharges through the load. This process repeats, providing a smoothed output waveform with minimal ripple.




### (ii) Choke input filter:

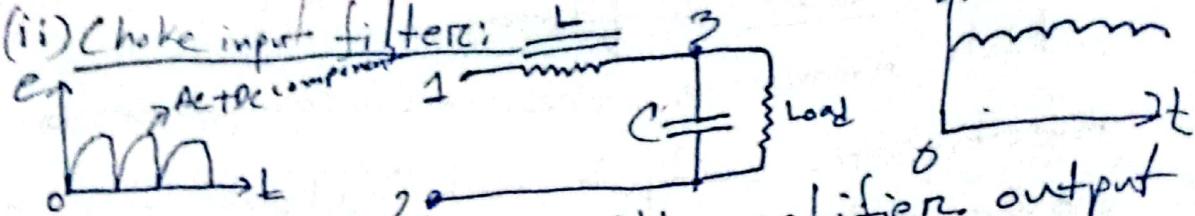

- Choke L in series with rectifier output and filter capacitor (C) across the load.
- Choke opposes AC but allows DC to pass, reducing pulsations.
- Most AC appears across choke, while DC passes through the load.
- Filter capacitor bypasses remaining AC, allowing only DC to reach the load.
- Provides a smoother DC output.

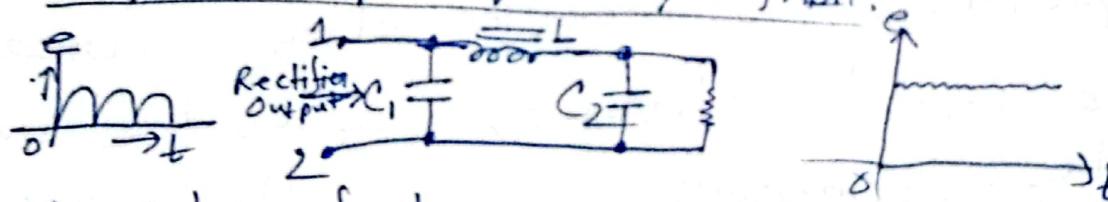
### (iii) Capacitor input filter / pi-filter:



- Consists of two filter capacitors C1 across rectifier output, choke(L) in series, and another filter cap C2 across the load.
- C1 bypasses AC, allowing DC to reach the choke.
- Choke allows DC to pass but blocks most AC.
- C2 bypasses remaining AC, allowing only DC to appear across the load.
- Effective in reducing ripple and improving the smoothness of the output voltage.

Zener Diode: A properly doped crystal diode which has a sharp breakdown voltage is known as a zener diode.  $\square$

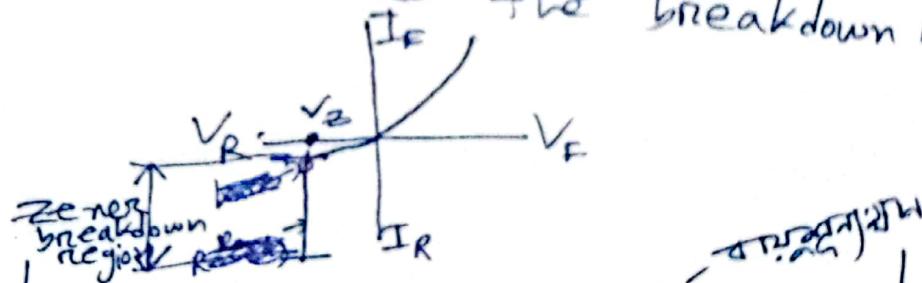- i) A zener diode is like an ordinary diode except that it is properly doped so have a sharp breakdown voltage.
- ii) A zener diode is always reverse connected Biased.
- iii) A " " has sharp breakdown voltage, are called zener voltage  $V_Z$ .
- iv) When forward biased, its characteristics are just ~~like~~ those of ordinary diode.
- v) The zener diode is not immediately burnt because it has entered the breakdown region.



Crystal diode versus vacuum vacuum diode


- Crystal diode have a number of advantages and disadvantages compared to vacuum diode;
- Advantages:
- i) They are smaller, more rugged and have a longer life.
  - ii) They are cheaper and inherently cheap.
  - iii) They require no filament power. As a result they produce less heat than vacuum diode.

## Disadvantages:


- ① Extremely heat-sensitive
- ② i) Limited temperature range; excess heat can damage the PN junction.
- ③ Handle smaller currents and low inverse voltages compared to vacuum diode
- ④ They cannot stand an overload even for a short period.
- ⑤ Vacuum diode can withstand a wide range of temperature changes.
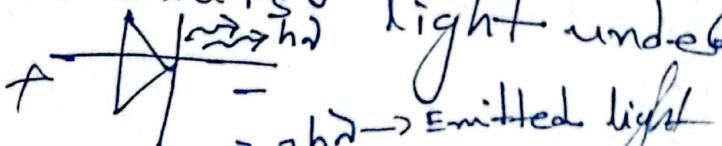
## LED

Light Emitting Diode: It is heavily doped P,N junction diode which converts electrical energy into light energy. This diode emits light under forward biasing.



Working:

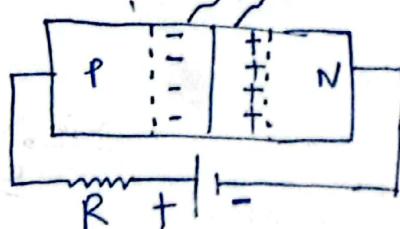

When PN junction is forward biased, electron and holes move towards opposite side of junction. Therefore, excess minority carriers on the either side of junction boundary, recombine with majority carriers near the junction. On the recombination of  $e^-$  and hole, the energy is given out in the form of light. The released energy is nearly equal to energy gap.


$$Eg = hn$$

Advantages of LED:

- (i) Low voltage
- (ii) Longer life (more than 20 years)
- (iii) less power consume
- (iv) Cheap and easy to handle.
- (v) low operational voltage.

(vi) Fast-on of switching.

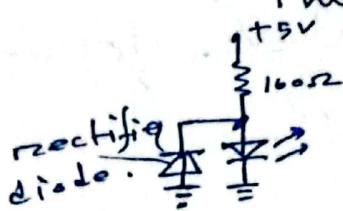(vii) Protecting LED against reverse bias.  
~~That is one way to protect a LED is to connect A rectifier diode in parallel with LED. This protect the LED from damage~~



### Application of LEDs:

i) As a power indicator:

A LED can be used to indicate whether the power is on or off. When the switch  $S$  is closed, power flows through the load ~~and~~ applied to the load and current flows through the LED which lights, indicating the power is on.

ii) Seven-segment display:

Purpose: To display numerical digits (0-9) using a combination of seven LEDs.

Fig (i)

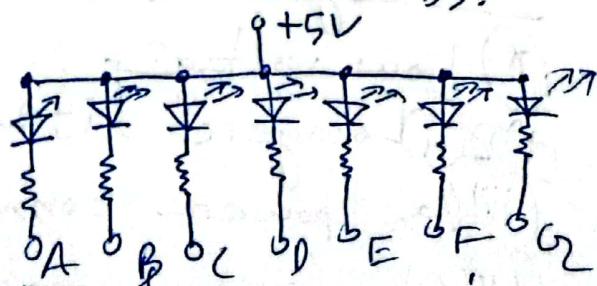


Fig (i) Shows ~~on~~ the front of a seven-segment


display. It contains seven LEDs (A, B, C, D, E, F, G). Each LED or segment lights up when forward biased. For example, lighting up A, B, C; D, G shows the number 3.

Fig(ii) shows the schematic diagram of seven-segment display. External series resistors connected to the anodes for safe current levels. Anode of all seven LEDs are connected to voltage +5V. This is known common-anode type. To light a specific LED, like A, we ground the point A, it forward biases the LED A which will be lit.

Q] What is photo diode? Explain the operating principle of photo diode with example and application.


Photo-diode: It is a device used to detect and convert light energy into electrical energy. It is operated under reverse bias below breakdown voltage.

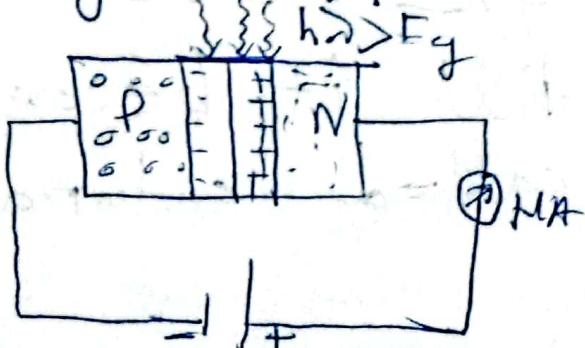Working: When the photodiode is illuminated with light, with energy greater than



energy gap of the semiconductor than that  $e^-$ -hole pairs are generated due to the absorption of photons. These charge carriers contribute to the reverse current.

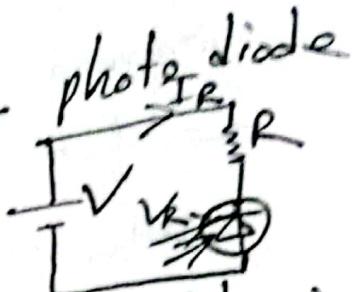
With example: Fig 6.1) show basic photo diode circuit.



- (i) the circuit has reverse-biased photo-diode. When no is incident in the pn junction of photo-diodes the reverse current  $I_{R}$  is extremely small this is called dark current.
- (ii) When light is incident <sup>on</sup> the pn junction of the photo diode, there is a transfer of energy (photons) to the atoms in the junction. This will create more free electrons and holes and increase reverse current.
- (iii) As the intensity <sup>of</sup> light increase the reverse current increased till it becomes maximum, this is called saturation current,

## VI Characteristics of photo-diode

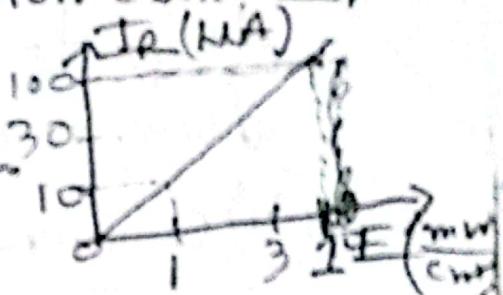- i) Reverse current - Illumination curve:
- The graph shows between reverse current ( $I_R$ ) and illumination ( $E$ ) of a photodiode.




$I_R$  is measured in mA and  $E$  is measured in  $mW/cm^2$ . Note the graph is a straight line passing through the origin.

$$I_R = mE \quad [m = \text{slope}]$$

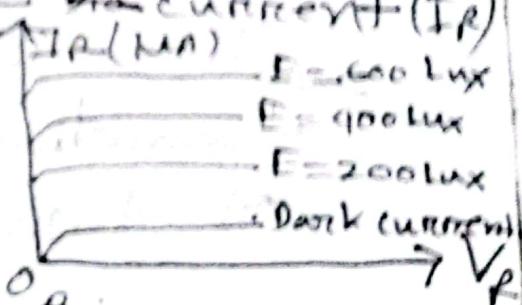- ii) Reverse voltage - Reverse current curve:

The graph between reverse bias current ( $I_R$ ) and reverse voltage ( $V_R$ ).


It is cleared that for a given reverse biased voltage  $V_R$ , the reverse current  $I_R$  increases.



### Applications of Photo-diode:

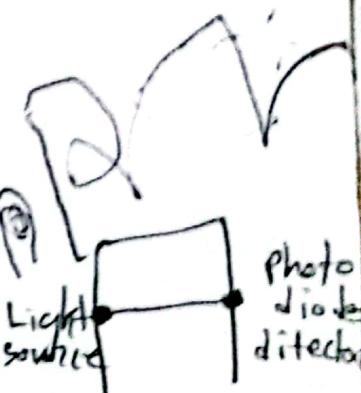- i) Alarm circuit using photo diode:

Light from a light source fall on a photo diode fitted. The reverse current  $I_R$  will continue to flow as long as the light beam is not broken. If a



person passes through the door, light beam is broken and the reverse current drops to the dark level current and an alarm is sounded.

(ii) Counter circuit using photo-diode: A photo diode may be used to count items on a conveyor belt. If an object passes through the conveyor belt, light beam is broken. It drops to the dark current and the count is increased by one.

Q] What is tunnel diode? Explain the tunneling effect and VI characteristics of tunnel diode.